



K17U 1071

Reg. No.:

Name :

II Semester B.C.A. Degree (CBCSS – Reg./Supple./Imp.)

Examination, May 2017

Core Course

2B02 BCA : DIGITAL SYSTEMS

(2014 Admn. Onwards)

Time : 3 Hours

Max. Marks : 40

SECTION – A

1. One word answer.

(8×0.5=4)

- If the input to a NOT gate is A and the output is X then $X =$ _____
- The Boolean expression $\overline{A}B(A + \overline{B})$ can be reduced to _____
- The NAND gate output will be low if the two inputs are _____
- BCD is _____
- The decimal equivalent of hexa number 1A53 is _____
- When simplified with Boolean Algebra $(x + y)(x + z)$ simplifies to _____
- How many select lines will a 16 to 1 multiplexer will have _____
- For JK flip-flop with $J = 1, K = 0$ the output after clock pulse will be _____

SECTION – B

Write short notes on any seven of the following questions.

(7×2=14)

- Define Boolean Algebra.
- Which are the basic logic gates ?
- Define a register.
- What are decade counters ?
- Give the truth table of S-R and D-flip-flops.

P.T.O.



7. Define parity generator and parity checker.
8. Which are the different types of ROMs ?
9. What are parallel counters ?
10. Convert $(350)_8$ to hexadecimal and $(ABC)_{16}$ to octal.
11. Explain full adders.

SECTION – C

Answer **any four** of the following questions.

(4×3=12)

12. Explain Asynchronous counters.
13. What is a universal gate ? Give examples.
14. What is a Shift Register ? Which are the various types of Shift Registers ? List out some applications of Shift Register.
15. What are triggering of flip-flops ? Explain edge triggered flip-flops.
16. What is an encoder ? Explain an 8×3 encoder.
17. Explain GRAY code and UNICODE.

SECTION – D

Write an essay on **any two** of the following questions.

(2×5=10)

18. Using a suitable logic diagram explain the working of a 1-to-16 de multiplexer.
19. Simplify the function using K-map $f(w, x, y, z) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$.
20. What are combinational circuits ? Explain different types of combinational circuits with truth table and logic diagram.
21. What are flip-flops ? Explain any three flip-flops with truth table and logic diagram.